

THE UNIVERSITY OF DANANG
UNIVERSITY OF SCIENCE AND TECHNOLOGY
Faculty of Advanced Science and Technology



REPORT PROJECT

DESIGN OF DIGITAL CIRCUITS
AND SYSTEMS
TOPIC: TIMER

Instructor : Huynh Viet Thang
Class : 21ECE
Group : 3
Group members : Luong Nhu Quynh
Vo Van Buu
Tran Hoang Minh
Nguyen Thi Tam

Da Nang, December 26 th 2024

Contents

| | |
|--|----|
| Requirement..... | 3 |
| I. Block diagram..... | 4 |
| II. State diagram | 5 |
| III. Code Verilog..... | 6 |
| IV. Simulation result (ModelSIM)..... | 15 |
| V. Conclusion | 19 |
| 1. Project application | 19 |
| 2. Advantages and disadvantages | 20 |
| 3. Future Work and Development Potential of the Projec | 21 |
| Future work:..... | 21 |
| Development Potential of the Project: | 21 |
| VI. Reference | 22 |
| VII. Appendix..... | 22 |
| 1. Module: FSM_timer_minsec | 22 |
| Code: | 22 |
| Testbench: | 26 |
| 2. Module: timer60 : | 31 |
| Code: | 31 |
| Testbench: | 33 |
| Results:..... | 36 |
| 3. timer10..... | 36 |
| Code: | 36 |
| Testbench: | 44 |
| Results:..... | 47 |
| 4. Module frequency_1hz | 48 |
| Code: | 48 |

| | |
|------------------------------|----|
| Testbench: | 49 |
| Results:..... | 50 |
| 5. Module led_7_segment..... | 51 |
| Code: | 51 |
| Testbench: | 52 |
| Results:..... | 53 |
| 6. Module led_blinker..... | 54 |
| Code: | 54 |
| Testbench: | 54 |
| Results:..... | 56 |

Requirement

Design a timer circuit for the following purposes:

- Countdown: The timer should count down from an initial time set by the user to zero, then stop and provide an indication.
- Display: Display minutes and seconds elapsed on 4 seven-segment LEDs (2 LEDs for minutes, 2 LEDs for seconds).
- Alarm: When the countdown reaches zero, trigger an alarm by blinking an LED (dot or seven-segment).
- User input: Allow the user to set the initial countdown time (in minutes) using switches.
- Pause/resume: Enable the user to pause and resume the countdown.
- Reset: Allow the user to reset the timer, returning the display to the initial set time.
- Customization: Students can customize the design as desired to achieve the best results.

I. Block diagram

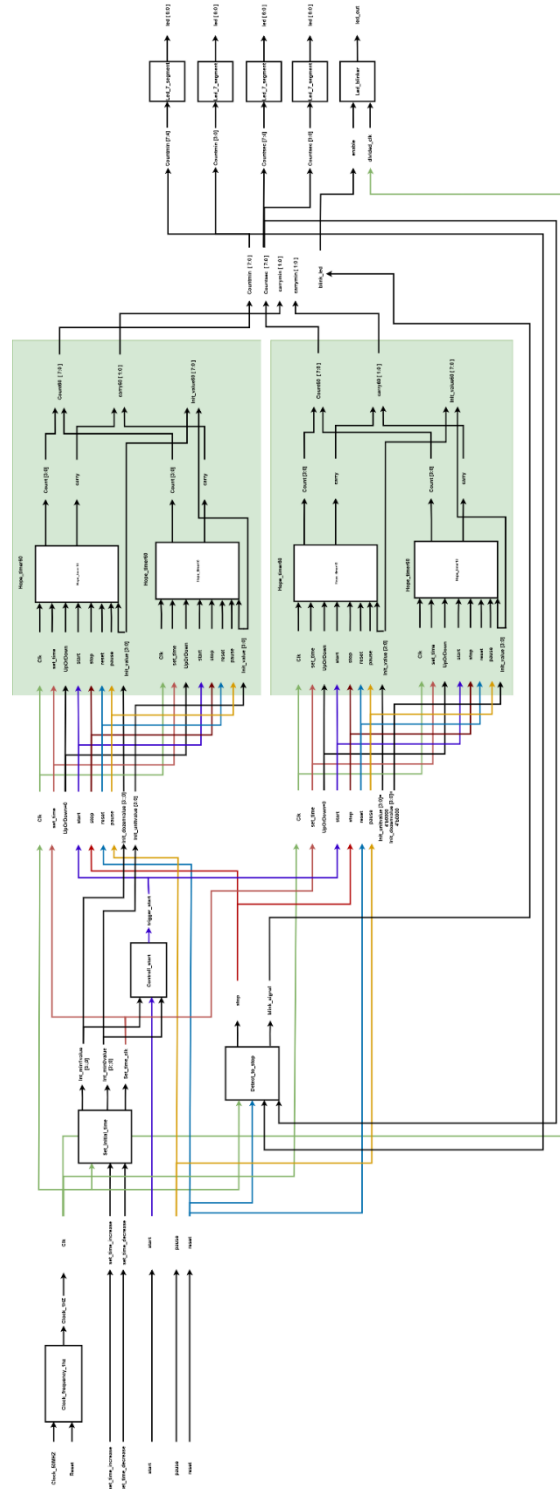


Fig 1. Block diagram of the timer

II. State diagram

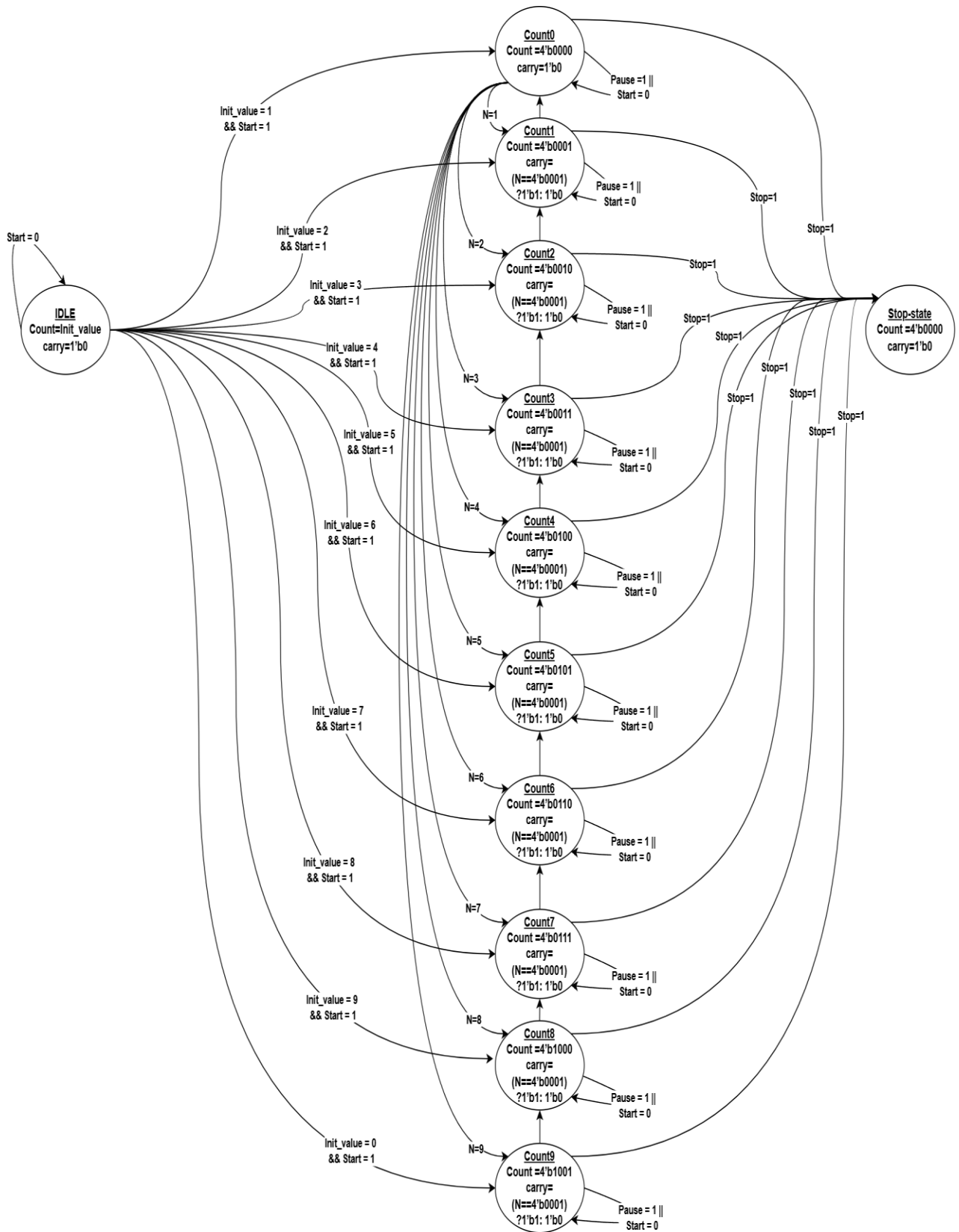


Fig 2. State diagram of the counter

III. Code Verilog

```
module FSM_timer_final

(

    input wire sys_clk,

    input wire set_time_increase,

    input wire set_time_decrease,

    input wire start,

    input wire pause,

    input wire reset,

    output wire [6:0] min1_led,

    output wire [6:0] min0_led,

    output wire [6:0] sec1_led,

    output wire [6:0] sec0_led,

    output wire blink_led

);

wire clk_1hz;

wire [7:0] Init_minvalue ;

wire [7:0] Init_secvalue ;

wire [7:0] Countmin ;

wire [7:0] Countsec ;
```

```

wire [1:0] carrymin ;

wire [1:0] carrysec ;

wire enable_led ;


// Create the clock 1 Hz for realtime timer

frequency_1hz Clk_block (.clk_in(sys_clk),.reset(reset),.clk_out(clk_1hz));

// Create the timer

FSM_timer_minsec FPGA_timer (

    .Clk(clk_1hz),

    .set_time_increase(set_time_increase),

    .set_time_decrease(set_time_decrease),

    .start(start),

    .pause(pause),

    .reset(reset),

    .Init_minvalue(Init_minvalue),

    .Init_secvalue(Init_secvalue),

    .Countmin(Countmin),

    .Countsec(Countsec),

    .carrymin(carrymin),

    .carrysec(carrysec),

```



```

        .blink_led(enable_led)

);

// Decode Output Count for display with 7 segment led

led_7_segment leg1_min (

    .bcd(Countmin[7:4]),

    .led(min1_led)

);

led_7_segment leg0_min (

    .bcd(Countmin[3:0]),

    .led(min0_led)

);

led_7_segment leg1_sec (

    .bcd(Countsec[7:4]),

    .led(sec1_led)

);

led_7_segment leg0_sec (

    .bcd(Countsec[3:0]),

    .led(sec0_led)

);

// Blink led when the timer is finished...

```

```

led_blinker toggle_led (

    .divided_clk(clk_1hz),

    .enable(enable_led),

    .led_out(blink_led)

);

endmodule

```

– Code Verilog Testbench

```

`timescale 1ns / 1ns

module FSM_timer_final_tb ;

localparam T = 20; //( T=20ns )

reg sys_clk;

reg set_time_increase;

reg set_time_decrease;

reg start;

reg pause;

reg reset;

wire [6:0] min1_led;

wire [6:0] min0_led;

wire [6:0] sec1_led;

wire [6:0] sec0_led;

wire blink_led;

```

```

FSM_timer_final dut (

    .sys_clk(sys_clk),

    .set_time_increase(set_time_increase),

    .set_time_decrease(set_time_decrease),

    .start(start),

    .pause(pause),

    .reset(reset),

    .min1_led(min1_led),

    .min0_led(min0_led),

    .sec1_led(sec1_led),

    .sec0_led(sec0_led),

    .blink_led(blink_led)

);

// Clock generation with T=20 ns

always begin

    sys_clk = 1'b1;

    #(T / 2);

    sys_clk = 1'b0;

    #(T / 2);

end

```

```

// Reset logic

initial begin

    reset = 1'b0;

    pause = 1'b0;

    start = 1'b0;

    set_time_increase = 1'b1;

    set_time_decrease = 1'b1;

// 1s correspond with 50000000*T

    #(50000000*T);

end

initial

begin

    #(25000000*T);

// Increase initial time

set_time_increase = 1'b0;

    #(50000000*T);

set_time_increase = 1'b1;

    #(50000000*T);

set_time_increase = 1'b0;

    #(50000000*T);

set_time_increase = 1'b1;

```

```

#(500000000*T);

// decrease initial time

set_time_decrease = 1'b0;

#(500000000*T);

set_time_decrease = 1'b1;

#(500000000*T);

set_time_decrease = 1'b0;

#(500000000*T);

set_time_decrease = 1'b1;

#(500000000*T);

// Test decreases initial time when initial time = 0;

set_time_decrease = 1'b0;

#(500000000*T);

set_time_decrease = 1'b1;

#(500000000*T);

set_time_decrease = 1'b0;

#(500000000*T);

set_time_decrease = 1'b1;

#(1000000000*T);

// Increase initial time to 1 minute

set_time_increase = 1'b0;
```

```

#(500000000*T);

set_time_increase = 1'b1;

#(500000000*T);

//Running counter

start = 1'b1;

#(2500000000*T);

// Test set initial time when the timer is starting

set_time_increase = 1'b0;

#(500000000*T);

set_time_increase = 1'b1;

#(500000000*T);

set_time_decrease = 1'b0;

#(500000000*T);

set_time_decrease = 1'b1;

#(500000000*T);

// Test Pause function

pause=1'b1;

#(1000000000*T);

// Continousing counting

pause=1'b0;

#(64'd3000000000*T);

```

```
// Test increasing initial time when timer stopped
```

```
set_time_increase = 1'b0;
```

```
 #(500000000*T);
```

```
set_time_increase = 1'b1;
```

```
 #(500000000*T);
```

```
set_time_increase = 1'b0;
```

```
 #(500000000*T);
```

```
set_time_increase = 1'b1;
```

```
 #(1000000000*T);
```

```
// Stop timer and turn off blink leb by resetting
```

```
start=1'b0;
```

```
 #(500000000*T);
```

```
reset=1'b1;
```

```
 #(500000000*T);
```

```
reset=1'b0;
```

```
 #(500000000*T);
```

```
// Start Timer again
```

```
start=1'b1;
```

```
 #(1000000000*T);
```

```
// Test timer start =0 when timer is counting
```

```

start=1'b0;

#(100000000*T);

// Start timer again

start=1'b1;

#(200000000*T);

// Test reset to the initial time function

reset=1'b1;

#(100000000*T);

reset=1'b0;

// Finish timer

#(50000000*T);

$finish; // End simulation

end

endmodule

```


IV. Simulation result (ModelSIM)

| Segments (✓ = ON) | | | | | | | Display | Segments (✓ = ON) | | | | | | | Display |
|-------------------|---|---|---|---|---|---|---------|-------------------|---|---|---|---|---|---|---------|
| a | b | c | d | e | f | g | | a | b | c | d | e | f | g | |
| ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | | 0 | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | ✓ | 8 |
| | ✓ | ✓ | | | | | 1 | ✓ | ✓ | ✓ | | | ✓ | ✓ | 9 |
| ✓ | ✓ | | ✓ | ✓ | | ✓ | 2 | ✓ | ✓ | ✓ | | ✓ | ✓ | ✓ | A |
| ✓ | ✓ | ✓ | ✓ | | | ✓ | 3 | | | ✓ | ✓ | ✓ | ✓ | ✓ | b |
| | ✓ | ✓ | | | ✓ | ✓ | 4 | ✓ | | | ✓ | ✓ | ✓ | | c |
| ✓ | | ✓ | ✓ | | ✓ | ✓ | 5 | | ✓ | ✓ | ✓ | ✓ | | ✓ | d |
| ✓ | | ✓ | ✓ | ✓ | ✓ | ✓ | 6 | ✓ | | | ✓ | ✓ | ✓ | ✓ | E |
| ✓ | ✓ | ✓ | | | | | 7 | ✓ | | | | ✓ | ✓ | ✓ | F |


Table 1: The output of 7-segment commoning anode led corresponding with numbers

| Number | Decoded number |
|--------|----------------|
| 0 | 1111110 |
| 1 | 0110000 |
| 2 | 1101101 |
| 3 | 1111001 |
| 4 | 0110011 |
| 5 | 1011011 |
| 6 | 1011111 |
| 7 | 1110000 |
| 8 | 1111111 |
| 9 | 111101 |

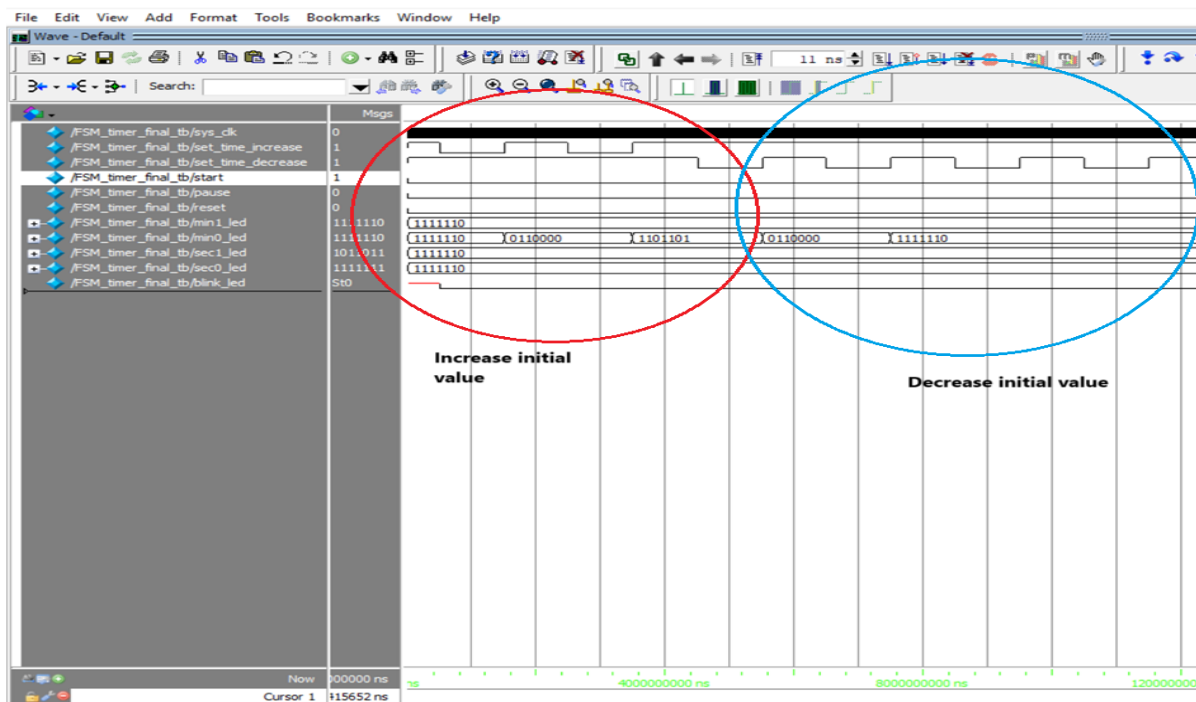
When set_increase_time is low at the positive edge, the initial time is increased by 1. Reversely, set_decrease_time is low at the positive edge of clock, the initial time is decreased by 1, and if initial time is 0, we can not continuously decrease.




Start to count, from 00:59 to 00:50

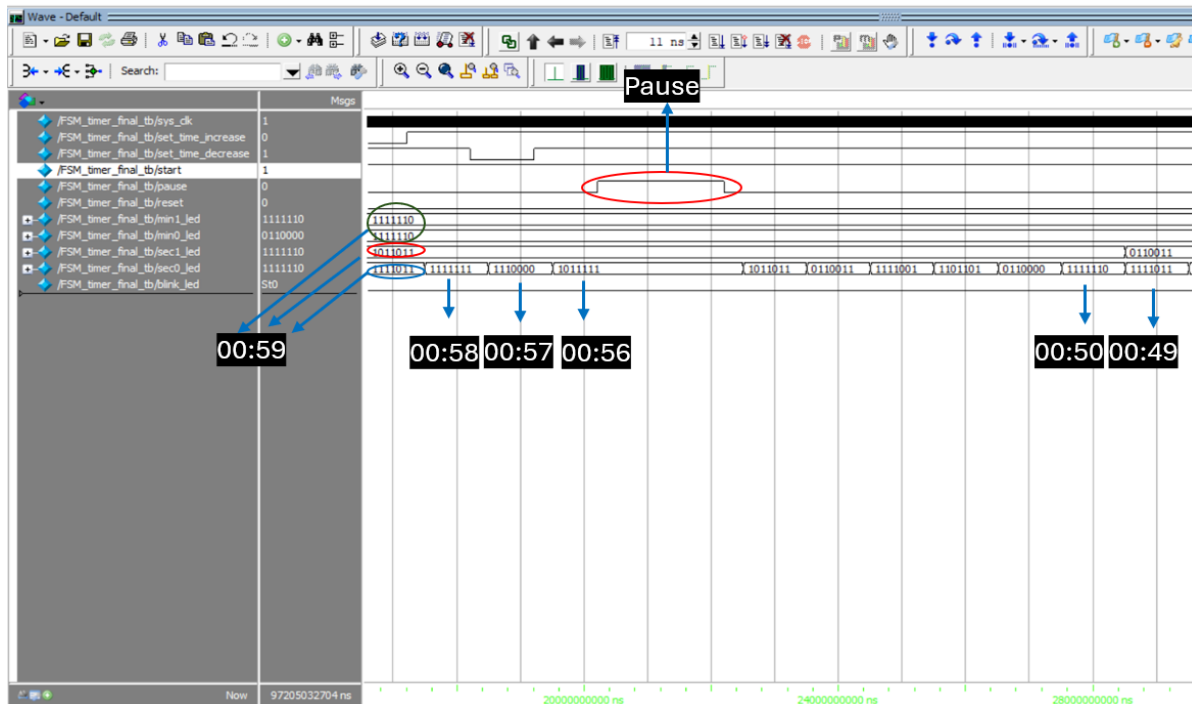


Count from 00:39 to 00:30

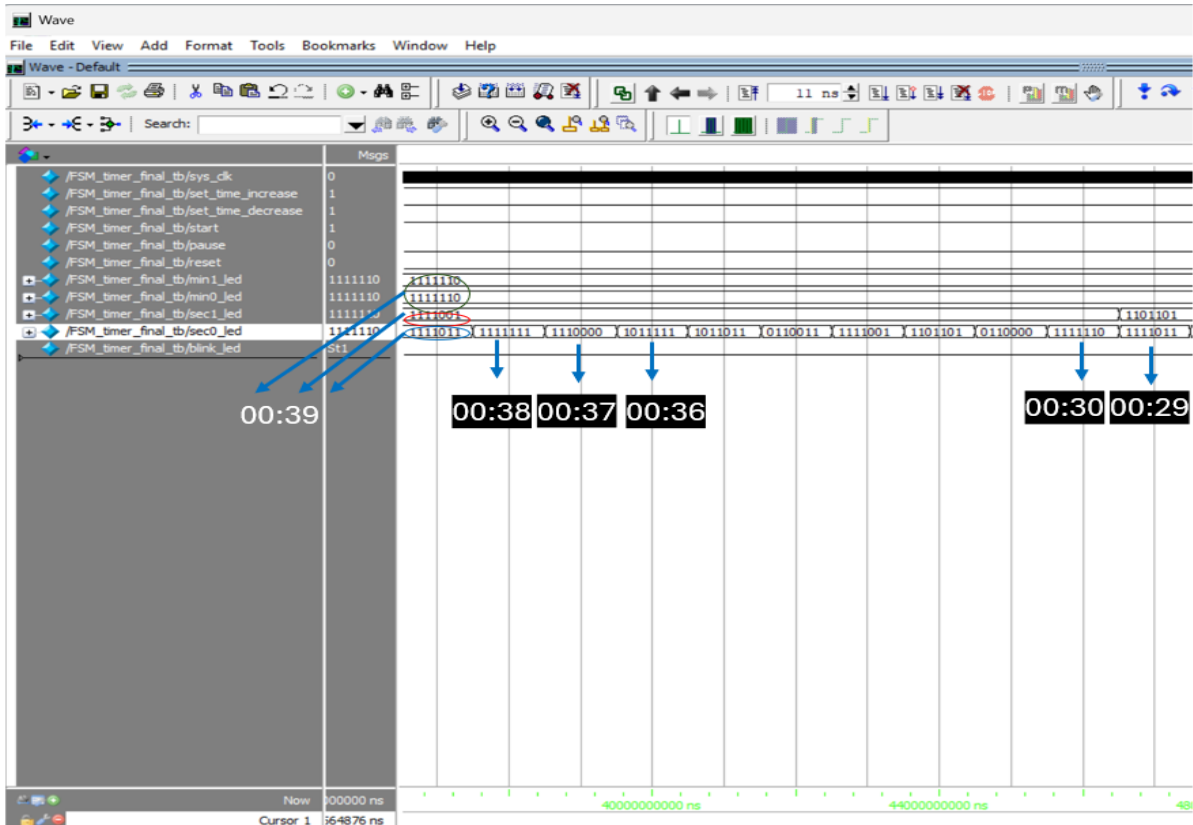


Count from 00:29 to 00:20

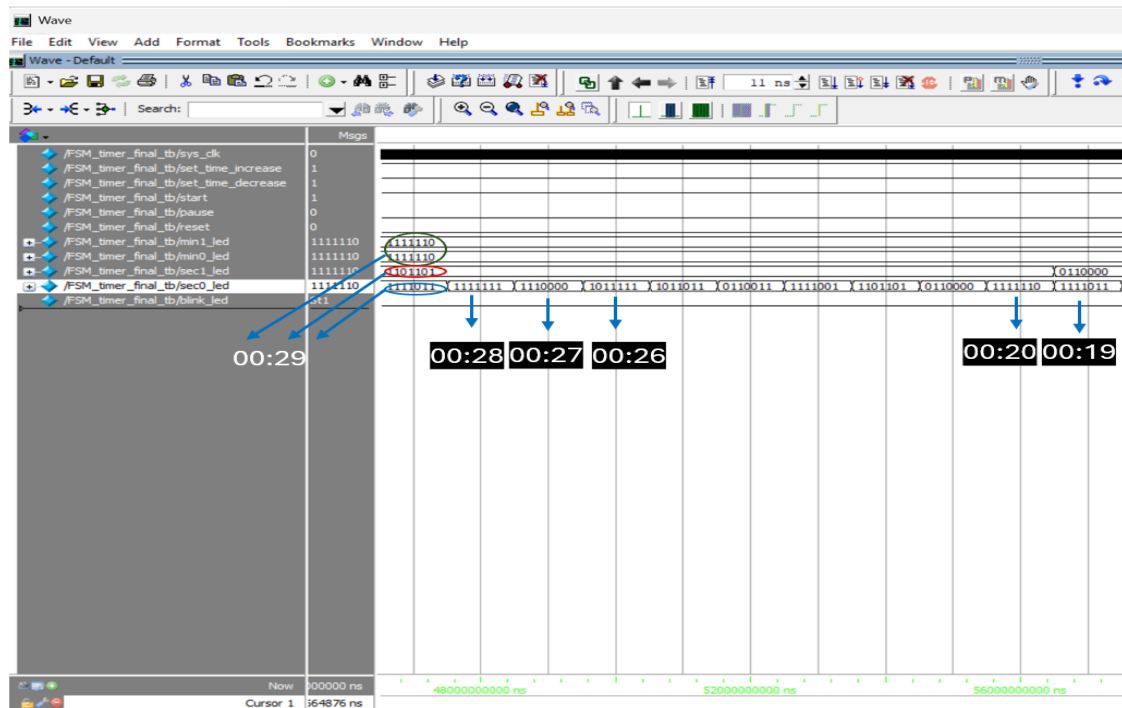

Count from 00:19 to 00:10

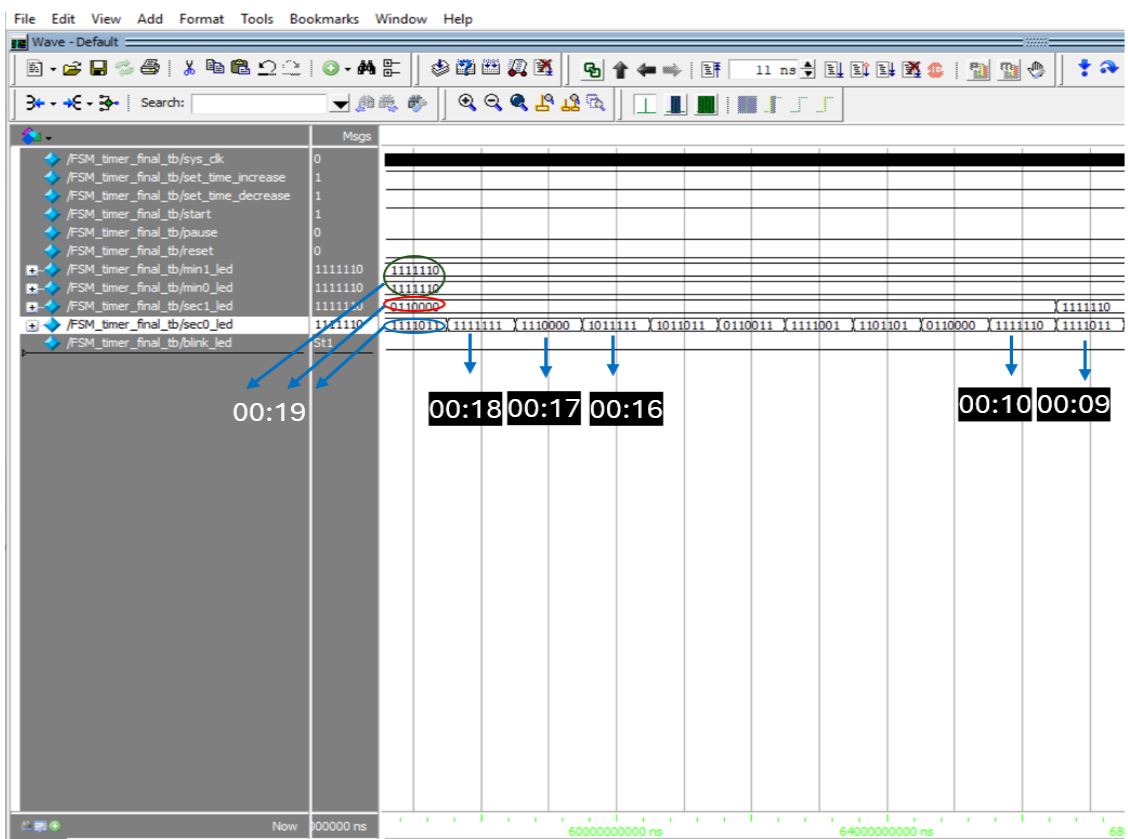


Count from 00:09 to 00:00

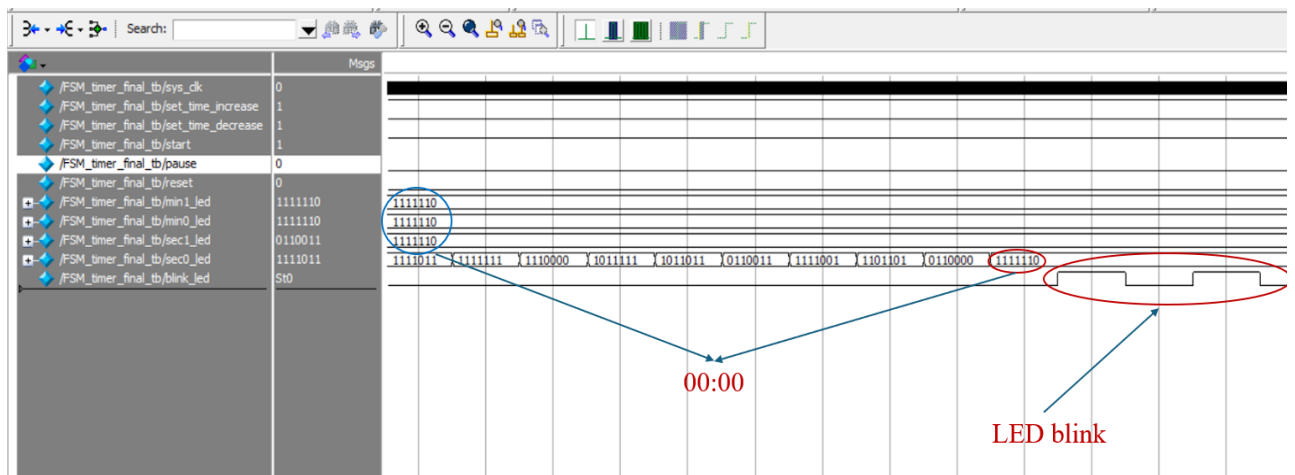

The timer enters the Pause state when the system counts and the user turns off the Start switch.

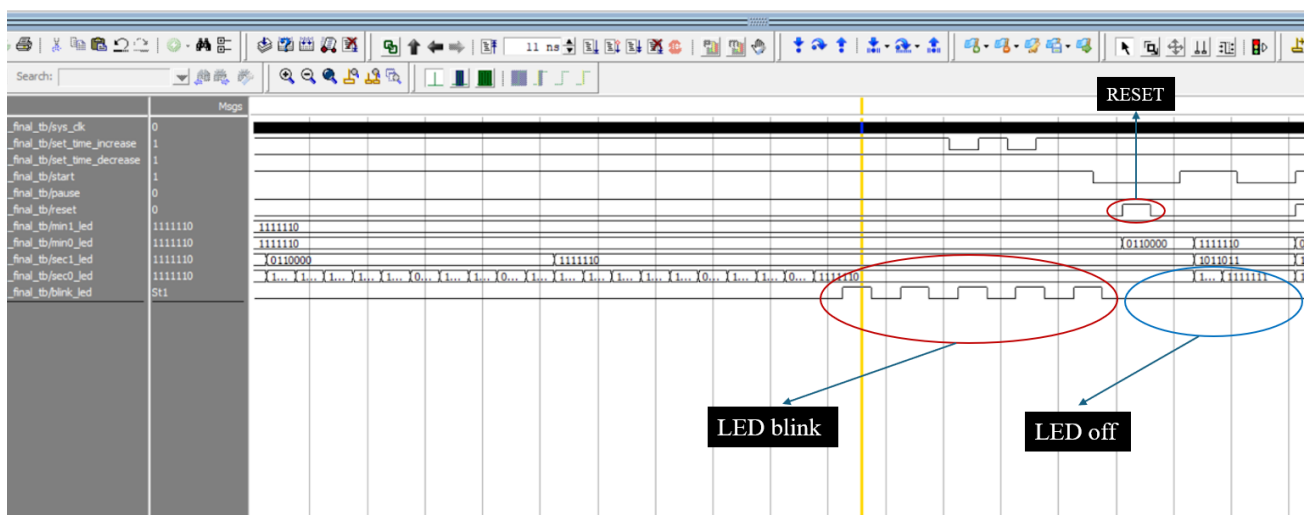When the system counts down to 0, the LED blinks. The system is in a Stop state (cannot increase or decrease the value) until the user resets the timer to the initial value.



V. Conclusion

1. Project application

Common Applications:

- Household:
 - Timer functions in microwaves, rice cookers, washing machines, and other household appliances.

- Alarms or time reminders in portable devices.
- Industrial:
 - Timing processes in production lines, measuring intervals between stages.
 - Countdown to automatically turn devices on/off or schedule periodic maintenance.
- Transportation: Countdown timers in traffic lights to help drivers and pedestrians prepare for changes in signals.
- Education and Sports: Timing during exams or sports activities.
- Special Applications:
 - Security devices such as timed locks...
 - Controlling events like motor activation or controlled industrial explosions.

2. Advantages and disadvantages

Advantages:

- The timer is a combination of sub-modules, with a 10-count module, the maximum value of the counter can change from 0 to 9, so it can be applied to combine into different counting values such as 99, 12, and 24... for use in many other applications.
- .The timer can increase or decrease the initial time by holding down or pressing and releasing to help adjust the time easily, along with the logic setting during operation that does not allow the timer to be started when the initial time has not been set, the initial value cannot be increased or decreased while the timer is running, helping the timer not to be interrupted during operation, and when finished, it can only be reactivated when the timer is started and reset is turned off, otherwise, it will not perform any other operations, always helping to signal the user until they perform the shutdown operation.

Disadvantages:

The timer is not optimal yet. Using multiple states for counting is a waste of resources and can cause conflicts in output values. Using two separate switches for start and pause, although it is possible to use only one which is also fine.

3. Future Work and Development Potential of the Project

Future work:

- Enhancing the optimization of the timer: Simplify counting states to save resources and minimize output value conflicts.
- Integrating smart sensors: Combine the timer with sensors for temperature, light, or motion to expand applications in smart homes and industries.
- Developing a user interface: Create an intuitive display or a mobile app for users to easily manage time settings.
- Increasing flexibility: Add more flexible timer functions, such as repeat timers or the ability to set multiple time intervals.
- Integrating IoT (Internet of Things): Connect the timer to other IoT devices to synchronize operations within an automation system.

Development Potential of the Project:

- Applications in smart homes: The timer can manage household devices like lights, air conditioners, heaters, fans, etc., helping to save energy and increase convenience.
- Development in the industrial sector: Applications in automated production lines, especially in industries requiring high precision, such as electronics, food, and beverage manufacturing.
- Applications in security: Use in security devices like automatic locks, smart doors, and fire alarm systems.
- Applications in education and sports: Develop devices to monitor time during competitions or sports training, improving accuracy and fairness.
- Integration with green energy: Develop timers powered by solar energy or other renewable energy sources to align with environmental protection trends.

VI. Reference

1. University of Washington. (2009). *Finite State Machines (FSM) [Lecture slides]*. Retrieved from <https://courses.cs.washington.edu/courses/cse370/09wi/LectureSlides/18-FSM.pdf>.
2. YouTube. (n.d.). *[CpE 100 Module 23: FSM Counters]*. YouTube. Retrieved December 26, 2024, from <https://www.youtube.com/watch?v=FmiyDP3O6ag>.
3. YouTube. (n.d.). *[VLSIE001] Bài 11 - Mô tả máy trạng thái (FSM) bằng Verilog]*. YouTube. Retrieved December 26, 2024, from <https://www.youtube.com/watch?v=I6TqiRhBank>.

VII. Appendix

1. Module: FSM_timer_minsec

Code:

```
module FSM_timer_minsec (  
    input wire Clk,  
    input wire set_time_increase,  
    input wire set_time_decrease,  
    input wire start,  
    input wire pause,  
    input wire reset,  
    output wire [7:0] Init_minvalue,  
    output wire [7:0] Init_secvalue,  
    output wire [7:0] Countmin,  
    output wire [7:0] Countsec,  
    output wire [1:0] carrymin,  
    output wire [1:0] carrysec,  
    output wire blink_led  
);  
  
// Internal registers  
reg [3:0] Int_min1value, Int_min0value;
```

```

reg [3:0] Int_sec1value, Int_sec0value;
reg blink_signal;

```

```

reg Set_clk;
reg stop;
wire trigger_start;
wire UpOrDown = 1'b0; // Always count down
// Initialization
initial begin
    Int_min1value = 4'b0000;
    Int_min0value = 4'b0000;
    Int_sec1value = 4'b0000;
    Int_sec0value = 4'b0000;
    stop = 1'b0;
    Set_clk = 1'b1;
    blink_signal = 1'b0;
end
assign blink_led = blink_signal;
assign trigger_start = (start && (!Int_min1value || !Int_min0value)) ? 1 : 0;
always @(posedge Clk) begin
    if (!start && !stop) begin
        if (set_time_increase==1'b0 ) begin
            if (Int_min0value < 4'b1001) begin
                Int_min0value <= Int_min0value + 1'b1;
            end else if (Int_min1value < 4'b0101) begin
                Int_min0value <= 4'b0000;
                Int_min1value <= Int_min1value + 1'b1;
            end else begin
                Int_min0value <= 4'b0000;
                Int_min1value <= 4'b0000;
            end
            Set_clk <= 1'b1;
        end else if (set_time_decrease==1'b0 ) begin

```



```

        if (Int_min0value > 4'b0000) begin
            Int_min0value <= Int_min0value - 1'b;
        end else if (Int_min1value > 4'b0000) begin
            Int_min1value <= Int_min1value - 1'b1;
            Int_min0value <= 4'b1001;
        end else begin
            Int_min1value <= 4'b0000;
            Int_min0value <= 4'b0000;
        end
        Set_clk <= 1'b1;
    end else begin
        Set_clk <= 1'b0;
    end
end
end

// Countdown logic and blink signal
always @(posedge Clk or posedge reset) begin
    if (reset) begin
        blink_signal <= 1'b0;
        stop <= 1'b0;
    end else if (trigger_start) begin
        if (Countmin==8'b00000000 && Countsec==8'b00000001 ) begin
            // Stop the timer when the countdown reaches zero
            blink_signal <= 1'b1;
            stop <= 1'b1;
        end
    end
end

// Second timer module
timer60 seccount (
    .Clk(Clk),
    .set_time(Set_clk),

```

```

        .UpOrDown(UpOrDown),
        .start(trigger_start),
        .stop(stop),
        .reset(reset),
        .pause(pause),
        .Init_unitvalue(Int_sec0value),
        .Init_dozenvalue(Int_sec1value),
        .Init_value60(Init_secvalue),
        .Count60(Countsec),
        .carry60(carrysec)
    );

    // Minute timer module
    timer60 mincount (
        .Clk(carrysec[1]),
        .set_time(Set_clk),
        .UpOrDown(UpOrDown),
        .start(trigger_start),
        .stop(stop),
        .reset(reset),
        .pause(pause),
        .Init_unitvalue(Int_min0value),
        .Init_dozenvalue(Int_min1value),
        .Init_value60(Init_minvalue),
        .Count60(Countmin),
        .carry60(carrymin)
    );

endmodule

```

Testbench:

```
module FSM_timer_minsec_tb;
localparam T = 20; // Clock period

// Inputs
reg clk;
reg set_time_increase;
reg set_time_decrease;
reg start;
reg reset;
reg pause;

// Outputs
wire [7:0] Init_minvalue;
wire [7:0] Init_secvalue;
wire [7:0] Countmin;
wire [7:0] Countsec;
wire [1:0] carrymin;
wire [1:0] carrysec;
wire blink_led;

// Instantiate the Unit Under Test (UUT)
FSM_timer_minsec uut (
.Clk(clk),
.set_time_increase(set_time_increase),
.set_time_decrease(set_time_decrease),
.start(start),
.pause(pause),
.reset(reset),
.Init_minvalue(Init_minvalue),
. Init_secvalue( Init_secvalue),
.Countmin(Countmin),
.Countsec(Countsec),
.carrymin(carrymin),
. carrysec(carrysec),
```

```

.blink_led(blink_led)
);

// Clock generation
always begin
clk = 1'b1;
#(T / 2);
clk = 1'b0;
#(T / 2);
end

// Reset logic
initial begin
reset = 1'b0;
pause = 1'b0;
start = 1'b0;
set_time_increase = 1'b1;
set_time_decrease = 1'b1;
#(T);
end
initial
begin

#(T/2);

// Increase initial time

set_time_increase = 1'b0;
#(T);
set_time_increase = 1'b1;
#(T);
set_time_increase = 1'b0;
#(T);

```

```

set_time_increase = 1'b1;
#(T);

// decrease initial time

set_time_decrease = 1'b0;
#(T);
set_time_decrease = 1'b1;
#(T);

set_time_decrease = 1'b0;
#(T);
set_time_decrease = 1'b1;
#(T);

// Test decreases initial time when initial time = 0;

set_time_decrease = 1'b0;
#(T);
set_time_decrease = 1'b1;
#(T);

set_time_decrease = 1'b0;
#(T);
set_time_decrease = 1'b1;
#(2*T);

// Increase initial time to 1 minute

set_time_increase = 1'b0;
#(T);
set_time_increase = 1'b1;
#(T);

```

```

//Running counter
start = 1'b1;
#(5*T);

// Test set initial time when the timer is starting

set_time_increase = 1'b0;
#(T);
set_time_increase = 1'b1;
#(T);

set_time_decrease = 1'b0;
#(T);
set_time_decrease = 1'b1;

#(T);
// Test Pause function
pause=1'b1;
#(2*T);
// Continousing counting
pause=1'b0;
#(55*T);
// Test increasing initial time when timer stopped
set_time_increase = 1'b0;
#(T);
set_time_increase = 1'b1;
#(T);
set_time_increase = 1'b0;
#(T);
set_time_increase = 1'b1;
#(2*T);
// Stop timer and turn off blink leb by resetting

```

```

start=1'b0;
#(T);
reset=1'b1;
#(T);
reset=1'b0;
#(T);

// Start Timer again
start=1'b1;
#(2*T);

// Test timer start =0 when timer is counting
start=1'b0;
#(2*T);

// Start timer again
start=1'b1;
#(4*T);

// Test reset to the initial time function
reset=1'b1;
#(2*T);
reset=1'b0;
// Finish timer
#(T);
$finish; // End simulation
end
endmodule

```

2. Module: timer60 :

Code:

```
module timer60 (  
    input wire Clk,  
    input wire set_time,  
    input wire UpOrDown,  
    input wire start,  
    input wire stop,  
    input wire reset,  
    input wire pause,  
    input wire [3:0] Init_unitvalue,  
    input wire [3:0] Init_dozenvalue,  
    output wire [7:0] Init_value60,  
    output wire [7:0] Count60,  
    output wire [1:0] carry60  
);  
  
    // Wires for lower and upper counters  
    wire [3:0] count_lower, count_upper;  
    wire carry_lower, carry_upper;  
  
    // Assign combined outputs  
    assign Init_value60 = {Init_dozenvalue, Init_unitvalue};  
    assign Count60 = {count_upper, count_lower};  
    assign carry60 = {carry_upper, carry_lower};  
  
    // Instantiate lower timer (Units)  
    timer10 #(.N(4'b1001)) Unit (  
        .Clk(Clk),
```



```

        .set_time(set_time),
        .start(start),
        .stop(stop),
        .reset(reset),
        .pause(pause),
        .UpOrDown(UpOrDown),
        .Init_value(Init_unitvalue),
        .Count(count_lower),
        .carry(carry_lower)
    );

    // Instantiate upper timer (Dozens) with carry_lower as clock
    timer10 #(.N(4'b0101)) Dozen ( // Dozen counter wraps at 5 (0–59 counting)
        .Clk(carry_lower), // Use carry_lower as clock
        .set_time(set_time),
        .start(start),
        .stop(stop),
        .reset(reset),
        .pause(pause),
        .UpOrDown(UpOrDown),
        .Init_value(Init_dozenvalue),
        .Count(count_upper),
        .carry(carry_upper)
    );
endmodule

```

Testbench:

```
module timer60_tb;

// Inputs

    reg Clk;

    reg set_time;

    reg UpOrDown;

    reg start;

    reg stop;

    reg reset;

    reg pause;

    reg [3:0] Init_unitvalue;

    reg [3:0] Init_dozenvalue;

// Outputs

    wire [7:0] Init_value60;

    wire [7:0] Count60;

    wire [1:0] carry60;

// Instantiate the Unit Under Test (UUT)

    timer60 uut (

        .Clk(Clk),

        .set_time(set_time),

        .UpOrDown(UpOrDown),

        .start(start),

        .stop(stop),

        .reset(reset),

        .pause(pause),

        .Init_unitvalue(Init_unitvalue),
```

```

        .Init_dozenvalue(Init_dozenvalue),
        .Init_value60(Init_value60),
        .Count60(Count60),
        .carry60(carry60)
    );

    // Clock generation

    initial begin

        Clk = 0;

        forever #5 Clk = ~Clk; // 10ns clock period

    end

    // Testbench logic

    initial begin

        // Initialize inputs

        set_time = 0;

        UpOrDown = 0; // Start with down-counting

        start = 0;

        stop = 0;

        reset = 0;

        pause = 0;

        Init_unitvalue = 4'b0101; // Initial value = 5 (units)

        Init_dozenvalue = 4'b0010; // Initial value = 2 (dozens)

        // Wait for global reset

        #20;

        // Set initial time

        set_time = 1;

        #10;

        set_time = 0;

```

```

// Start counting down

start = 1;

#100;

// Pause the timer

pause = 1;

#20;

pause = 0;

#50;

// Stop the timer

stop = 1;

#20;

stop = 0;

#30;

// Reset the timer

reset = 1;

#10;

reset = 0;

// Change to up-counting

UpOrDown = 1;

start = 1;

#200;

// Finish simulation

$stop;

end

// Monitor values

initial begin

```

```

$monitor("Time=%0t | Init_value60=%b | Count60=%b | carry60=%b | start=%b |
pause=%b | stop=%b | reset=%b",



$time, Init_value60, Count60, carry60, start, pause, stop, reset);

end

endmodule

```

Results:

  

3. timer10

Code:

```

module timer10

#(parameter N = 4'b1001) // Max count value

(

    input wire set_time,

    input wire Clk,

    input wire start,

```

```

input wire stop,

input wire reset,

input wire pause,

input wire UpOrDown, // High for UP counter, Low for DOWN counter

input wire [3:0] Init_value,

output reg [3:0] Count,

output reg carry

);

// State Definitions

localparam [3:0]

    Count0 = 4'b0000,

    Count1 = 4'b0001,

    Count2 = 4'b0010,

    Count3 = 4'b0011,

    Count4 = 4'b0100,

    Count5 = 4'b0101,

    Count6 = 4'b0110,

    Count7 = 4'b0111,

    Count8 = 4'b1000,

    Count9 = 4'b1001,

    IDE    = 4'b1010,

    Stop_state = 4'b1100;

reg [3:0] state_reg, state_next;

// Synchronous State Update

always @(posedge Clk or posedge reset or posedge set_time) begin

    if (reset || set_time)

        state_reg <= IDE;

```

```

else

    state_reg <= state_next;

end

// Combinational Next-State Logic

always @* begin

    state_next = state_reg;

    case (state_reg)

        IDE: begin

            if (start) begin

                if (UpOrDown)

                    state_next = (Init_value == N) ? Count0 : Init_value + 1'b1;

                else

                    state_next = (Init_value == 4'b0000) ? N : Init_value - 1'b1;

            end

        end

        end

    Count0: begin

        if (stop)

            state_next = Stop_state;

        else if (!start || pause)

            state_next = Count0;

        else

            state_next = UpOrDown ? Count1 : N;

        end

    Count1: begin

        if (stop)

            state_next = Stop_state;

        else if (!start || pause)

```

```

        state_next = Count1;

    else

        state_next = UpOrDown ? ((Count == N) ? Count0 : Count2) : Count0;
    end

Count2: begin

    if (stop)

        state_next = Stop_state;

    else if (!start || pause)

        state_next = Count2;

    else

        state_next = UpOrDown ? ((Count == N) ? Count0 : Count3) : Count1;
    end

Count3: begin

    if (stop)

        state_next = Stop_state;

    else if (!start || pause)

        state_next = Count3;

    else

        state_next = UpOrDown ? ((Count == N) ? Count0 : Count4) : Count2;
    end

Count4: begin

    if (stop)

        state_next = Stop_state;

    else if (!start || pause)

        state_next = Count4;

    else

        state_next = UpOrDown ? ((Count == N) ? Count0 : Count5) : Count3;

```



```

end

Count5: begin
    if (stop)
        state_next = Stop_state;
    else if (!start || pause)
        state_next = Count5;
    else
        state_next = UpOrDown ? ((Count == N) ? Count0 : Count6) : Count4;
    end
end

Count6: begin
    if (stop)
        state_next = Stop_state;
    else if (!start || pause)
        state_next = Count6;
    else
        state_next = UpOrDown ? ((Count == N) ? Count0 : Count7) : Count5;
    end
end

Count7: begin
    if (stop)
        state_next = Stop_state;
    else if (!start || pause)
        state_next = Count7;
    else
        state_next = UpOrDown ? ((Count == N) ? Count0 : Count8) : Count6;
    end
end

Count8: begin
    if (stop)

```

```

        state_next = Stop_state;

    else if (!start || pause)

        state_next = Count8;

    else

        state_next = UpOrDown ? ((Count == N) ? Count0 : Count9) : Count7;
end

Count9: begin

    if (stop)

        state_next = Stop_state;

    else if (!start || pause)

        state_next = Count9;

    else

        state_next = UpOrDown ? Count0 : Count8;

    end

    Stop_state: ; // No operation

    default: state_next = IDE;

endcase

end

// Output Logic

always @* begin

    carry = 1'b0;

    case (state_reg)

        IDE: Count = Init_value;

        Count0: begin

            Count = 4'b0000;

            carry = UpOrDown;

```

```

end

Count1: begin
    Count = 4'b0001;
    carry = (!UpOrDown && (Count == N));
end

Count2: begin
    Count = 4'b0010;
    carry = (!UpOrDown && (Count == N));
end

Count3: begin
    Count = 4'b0011;
    carry = (!UpOrDown && (Count == N));
end

Count4: begin
    Count = 4'b0100;
    carry = (!UpOrDown && (Count == N));
end

Count5: begin
    Count = 4'b0101;
    carry = (!UpOrDown && (Count == N));
end

Count6: begin
    Count = 4'b0110;
    carry = (!UpOrDown && (Count == N));
end

Count7: begin
    Count = 4'b0111;

```

```
        carry = (!UpOrDown && (Count == N));  
    end  
    Count8: begin  
        Count = 4'b1000;  
        carry = (!UpOrDown && (Count == N));  
    end  
    Count9: begin  
        Count = 4'b1001;  
        carry = (!UpOrDown);  
    end  
    Stop_state: begin  
        Count = 4'b0000;  
        carry = 1'b0;  
    end  
    default: begin  
        Count = 4'b0000;  
        carry = 1'b0;  
    end  
endcase  
end  
endmodule
```

Testbench:

```
`timescale 1ns / 1ps

module timer10_tb;

    // Inputs

    reg set_time;

    reg Clk;

    reg start;

    reg stop;

    reg reset;

    reg pause;

    reg UpOrDown;

    reg [3:0] Init_value;

    // Outputs

    wire [3:0] Count;

    wire carry;

    // Instantiate the Unit Under Test (UUT)

    timer10 uut (

        .set_time(set_time),

        .Clk(Clk),

        .start(start),

        .stop(stop),

        .reset(reset),

        .pause(pause),

        .UpOrDown(UpOrDown),

        .Init_value(Init_value),

        .Count(Count),
```

```

        .carry(carry)

    );

    // Clock generation

    always #5 Clk = ~Clk;

    // Test sequence

    initial begin

        // Initialize Inputs

        set_time = 0;

        Clk = 0;

        start = 0;

        stop = 0;

        reset = 0;

        pause = 0;

        UpOrDown = 0;

        Init_value = 4'b0000;

        // Reset the timer

        reset = 1;

        #10;

        reset = 0;

        #10;

        // Set initial value

        set_time = 1;

        Init_value = 4'b0101;

        #10;

        set_time = 0;

        #10;

        // Start counting up

```

```

start = 1;

UpOrDown = 1;

#50;

// Pause

pause = 1;

#20;

pause = 0;

#30;

// Stop counting

stop = 1;

#20;

stop = 0;

// Reset again

reset = 1;

#10;

reset = 0;

// Set initial value for countdown

set_time = 1;

Init_value = 4'b1001;

#10;

set_time = 0;

// Start counting down

start = 1;

UpOrDown = 0;

#50;

// Pause

pause = 1;

```

```

#20;

pause = 0;

#30;

// Stop counting

stop = 1;

#20;

stop = 0;

// End simulation



$stop;

end

endmodule

```

Results:

  

4. Module frequency_1hz

Code:

```
module frequency_1hz (  
    input wire clk_in,    // Input clock (50 MHz)  
    input wire reset,     // Reset signal  
    output reg clk_out    // Output clock (0.5s HIGH, 0.5s LOW) );  
    reg [25:0] counter; // 26-bit counter  
  
    initial  
    begin  
        clk_out = 1'b0;  
        counter = 26'd0;  
    end  
  
    always @(posedge clk_in or posedge reset) begin  
        if (reset) begin  
            counter <= 26'd0; // Reset the counter  
            clk_out <= 1'b0; // Reset the output clock  
        end else begin  
            if (counter == 26'd24999999) begin  
                counter <= 26'd0; // Reset the counter when it reaches 25 million  
                clk_out <= ~clk_out; // Toggle the output clock  
            end else begin  
                counter <= counter + 1'b1; // Increment the counter  
            end  
        end  
    end  
  
endmodule
```

Testbench:

```
`timescale 1ns/1ns // Define time unit and precision

module frequency_1hz_tb ;

    // Testbench signals

    reg clk_in;      // Input clock (simulating 50 MHz)

    reg reset;       // Reset signal

    wire clk_out;    // Output clock

    // Clock period for 50 MHz = 20 ns (1 / 50 MHz)

    localparam T= 20;

    // Instantiate the DUT (Device Under Test)

    frequency_1hz uut (

        .clk_in(clk_in),

        .reset(reset),

        .clk_out(clk_out)

    );

    // Generate a 50 MHz clock

    // Clock generation

    always begin

        clk_in = 1'b1;

        #(T / 2);

        clk_in = 1'b0;

        #(T / 2);

    end

    // Reset logic

    initial begin

        reset = 1'b0;
```

```

end

// Stimulus block with structured 'd' changes over time

initial

begin

    #(300000000*T);


    $finish; // End simulation

end

endmodule

```

Results:

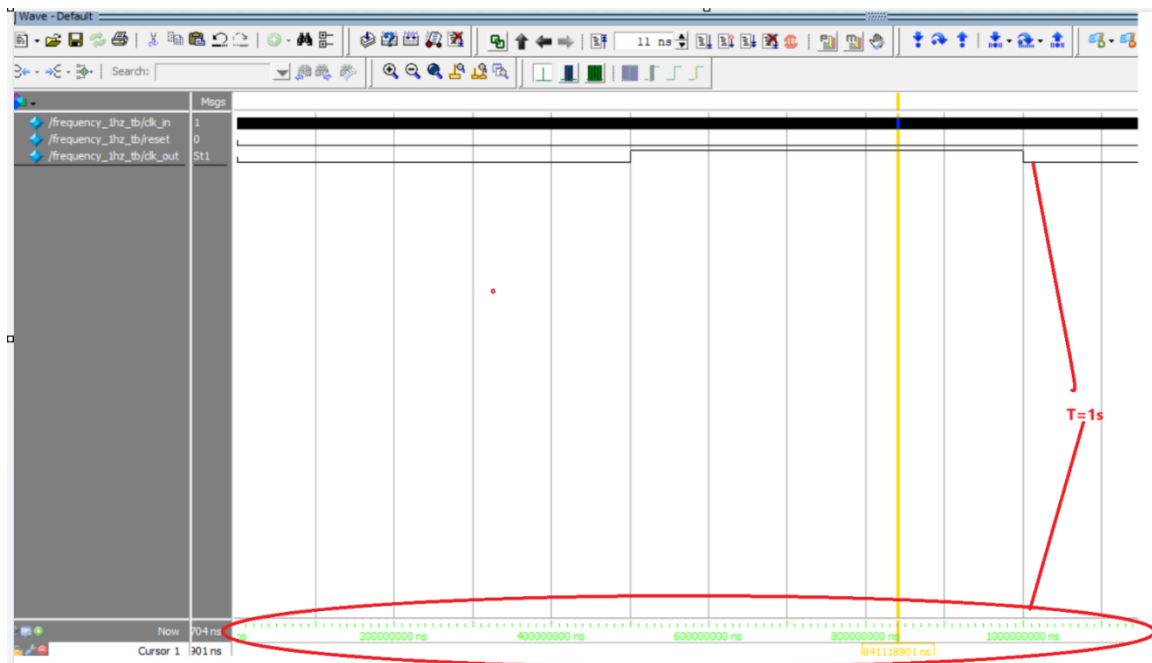

5. Module led_7_segment

Code:

```
module led_7_segment(  
    input [3:0] bcd, // Input 4-bit BCD  
    output reg [6:0] led // Output 7-bit LED segments  
);  
    always @(*) begin  
        case (bcd) // common anode  
            4'b0000: led = 7'b11111110; // 0  
            4'b0001: led = 7'b0110000; // 1  
            4'b0010: led = 7'b1101101; // 2  
            4'b0011: led = 7'b1111001; // 3  
            4'b0100: led = 7'b0110011; // 4  
            4'b0101: led = 7'b1011011; // 5  
            4'b0110: led = 7'b1011111; // 6  
            4'b0111: led = 7'b1110000; // 7  
            4'b1000: led = 7'b1111111; // 8  
            4'b1001: led = 7'b1111011; // 9  
            default: led = 7'b0000000; // Tắt LED nếu không hợp lệ  
        endcase  
    end  
endmodule
```

Testbench:

```
led_7_segment_tb.v

`timescale 1ns / 1ps

module led_7_segment_tb;

    reg [3:0] bcd;
    wire [6:0] led;

    led_7_segment dut (
        .bcd(bcd),
        .led(led)
    );

    initial begin
        bcd = 4'b0000;
        #10 bcd = 4'b0001;
        #10 bcd = 4'b0010;
        #10 bcd = 4'b0011;
        #10 bcd = 4'b0100;
        #10 bcd = 4'b0101;
        #10 bcd = 4'b0110;
        #10 bcd = 4'b0111;
        #10 bcd = 4'b1000;
        #10 bcd = 4'b1001;
        #10 bcd = 4'b1010; // Test default case
        #10 $finish;
    end
endmodule
```

```
end
```


```
always @(*) begin
```

```
    $display("Time: %0t, bcd: %b, led: %b", $time, bcd, led);
```

```
end
```

```
endmodule
```

Results:

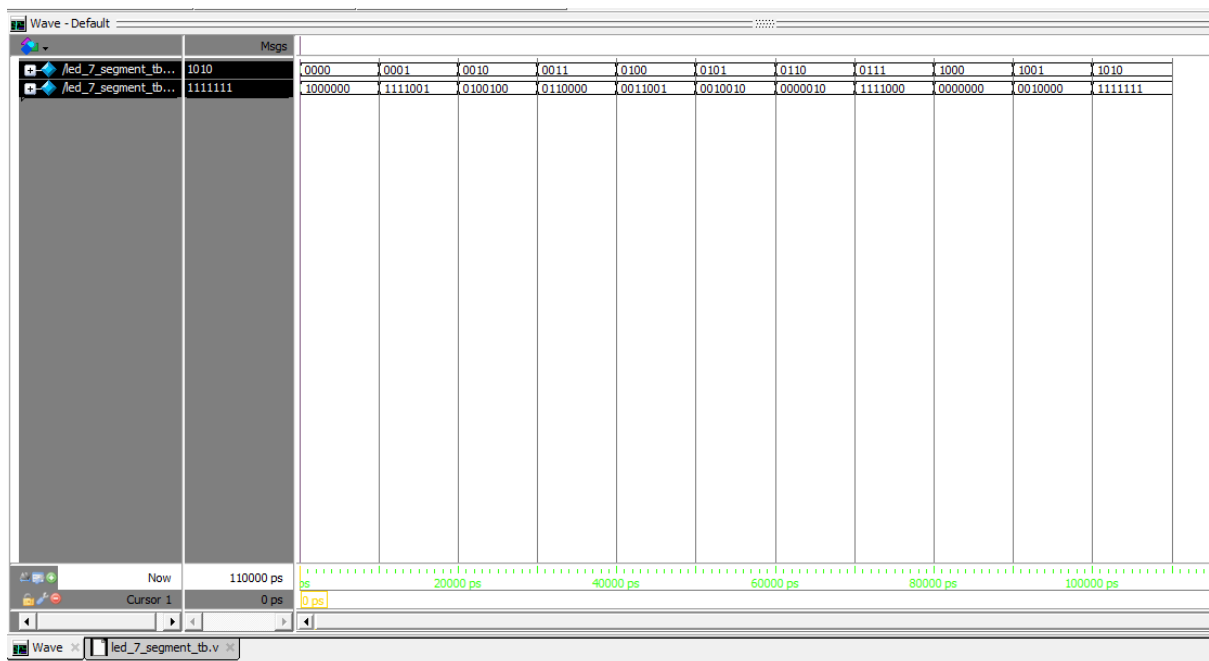

6. Module led_blinker

Code:

```
module led_blinker (  
    input wire divided_clk, // Input clock (already divided, e.g., 1 Hz)  
    input wire enable,      // Enable signal (1 = blink, 0 = off)  
    output reg led_out      // Output LED signal  
);  
  
always @(posedge divided_clk ) begin  
    if (enable) begin  
        led_out <= ~led_out; // Toggle LED when enabled  
    end else begin  
        led_out <= 1'b0; // Turn off LED when not enabled  
    end  
end  
  
endmodule
```

Testbench:

```
// Testbench for led_blinker module  
  
module led_blinker_tb;  
  
    // Testbench signals  
    reg divided_clk;  
    reg enable;  
    wire led_out;  
  
    // Instantiate the led_blinker module  
    led_blinker uut (  

```

```

        .divided_clk(divided_clk),

        .enable(enable),

        .led_out(led_out)
    );

    // Clock generation (simulating a 1 Hz clock)

    initial begin

        divided_clk = 0;

        forever #5 divided_clk = ~divided_clk; // 10 time units period
    end


    // Testbench process

    initial begin

        // Monitor signals for debugging

        $monitor($time, " divided_clk=%b, enable=%b, led_out=%b", divided_clk,
enable, led_out);


        // Initialize inputs

        enable = 0;


        // Test Case 1: LED off when enable = 0

        #20; // Wait for 2 clock cycles


        // Test Case 2: Enable blinking

        enable = 1;

        #100; // Wait for several clock cycles to observe LED toggling


        // Test Case 3: Disable blinking

```



```

enable = 0;

#20; // Wait for 2 clock cycles

// Test Case 4: Re-enable blinking

enable = 1;

#50; // Observe LED toggling again

// Test Case 5: Reset enable and observe LED off

enable = 0;

#30;

// Finish simulation

$stop;

end

endmodule

```

Results:

